

CSE 460: VLSI Design

Lab Experiment 2 (Blocking and Non-blocking Statements in Verilog)



Inspiring Excellence

Procedural Statements

- We learnt about “If Else” procedural statement in lab lecture 1.
 - This lecture we will learn about 2nd type procedural statement, the case statement.
- The bits in *expression* are called the *controlling expression*.
 - *Controlling expression* are checked for a match with each alternative.
 - The first successful match causes the associated statements to be evaluated.
 - Default case evaluates only when no other alternative matches.

```
case (expression)
  alternative1: begin
                    statement;
                end
  alternative2: begin
                    statement;
                end
  [default: begin
                statement;
            end]
endcase
```



Procedural Statements

- This is the code of 2 to 1 Mux using case statement.
- The mux can have two possible outputs because “s” is only 1 bit.
- Which is why the case statement has two alternatives.
- We could have included a default case because “s” can also have values of “x” and “z”. But we will learn about them soon.
- We can also use “1” as alternative instead of “1'b0”.
- If a statement in an alternative has multiple line it must be included in Begin-end block.

```
1 module mux2to1(w,s,f);
2
3   input [1:0]w;
4   input s;
5   output reg f;
6
7
8   always @(w or s)
9   =   case(s)
10      1'b0: f=w[0];
11      1'b1: f=w[1];
12   endcase
13
14 endmodule
```



Procedural Statements

```
1 module mux4to1(w,s,f);
2
3   input [3:0]w;
4   input [1:0]s;
5   output reg f;
6
7   always @(w,s)
8   =   case(s)
9       0: f=w[0];
10      1: f=w[1];
11      2: f=w[2];
12      3: f=w[3];
13      default: f=1'bx;
14   endcase
15 endmodule
```

S	00	01	10	11
f	W[0]	W[1]	W[2]	W[3]



Procedural Statements

- In the “case” statement , controlling bits can also have value of “x” and “z”.
- The values of “x” and “z” are also checked for exact match with the same values in the controlling expressions.
- The “case_x” statement treats both “x” and “z” as don’t cares.
- That means when they are present as input , code won’t check for their alternatives.
- In the right there is a Verilog code of priority encoder with 4 bit input “w” and output “y”.
- The first alternative “1xxx” specifies that if w[3] has the value of 1 , then the other inputs are treated as don’t cares and so the output is set to “y=3”

```
1 module prioenc(w,y);
2
3   input [3:0]w;
4   output reg[1:0]y;
5   |
6   always @(w)
7   =   casex (w)
8       4'b1xxx: y=3;
9       4'b01xx: y=2;
10      4'b001x: y=1;
11      4'b0001: y=0;
12      endcase
13 endmodule
```



Procedural Assignment Statements

- A value is assigned to a variable with a *procedural assignment statement*.
- There are two kinds of assignment statements.
 1. Blocking assignments
 2. Non-blocking assignments.
- Blocking assignments are denoted by the “=” symbol.
- Blocking means that first the assignment statement completes and updates it's left-hand side first.
- This updated left-hand side value is then used for evaluation of subsequent statements.

```
S = X + Y;  
p = S[0];
```



Procedural Assignment Statements

- At simulation time t_i the statements are evaluated in order.
- The first statement sets “ S ” to have the summation of current values of “ X ” and “ Y ” .
- Then the second statement sets “ p ” according to this current value of “ S ”

```
S = X + Y;  
p = S[0];
```



Inspiring Excellence


Procedural Assignment Statements

- 2nd types of assignment statement is non-blocking assignments.
- Non-blocking assignments use the “<=” symbol.
- At simulation time t_i the statements still are evaluated in order but they both use the value of the variables that exist at the start of simulation time.
- The first statement assigns a new value to “S” based on the current value of “X” and “Y” .
- But “S” is not actually changed to this value until all statements in the always block have been evaluated.
- For this , the value of “p” at time t_i is based on the value of “S” at time t_{i-1} .

```
S <= X + Y;  
p <= S[0];
```



Procedural Assignment Statements
  
```
module example7_3 (D, Clock, Q1, Q2);  
  input D, Clock;  
  output Q1, Q2;  
  reg Q1, Q2;  
  
  always @(posedge Clock)  
  begin  
    Q1 = D;  
    Q2 = Q1;  
  end  
  
endmodule
```



Procedural Assignment Statements

```
module example7_4 (D, Clock, Q1, Q2);  
  input D, Clock;  
  output Q1, Q2;  
  reg Q1, Q2;  
  
  always @(posedge Clock)  
  begin  
    Q1 <= D;  
    Q2 <= Q1;  
  end  
  
endmodule
```




Procedural Assignment Statements

```
1 module shiftreg(d,load,clk,q);
2
3     input [3:0]d;
4     input load,clk;
5     output reg[3:0]q;
6
7     always @(posedge clk)
8         if (load)
9             q<=d;
10        else
11            begin
12                q[3]<=q[0];
13                q[2]<=q[3];
14                q[1]<=q[2];
15                q[0]<=q[1];
16            end
17 endmodule
```

	q[3]	q[2]	q[1]	q[0]
initial	1	0	0	1
1 st cycle	1	1	0	0
2 nd cycle	0	1	1	0
3 rd cycle	0	0	1	1
4 th cycle	1	0	0	1



 Procedural Assignment Statements (Non-Blocking)



Procedural Assignment Statements


```
1 module shiftreg(d,load,clk,q);
2
3     input [3:0]d;
4     input load,clk;
5     output reg[3:0]q;
6
7     always @(posedge clk)
8         if (load)
9             q<=d;
10        else
11            begin
12                q[3]=q[0];
13                q[2]=q[3];
14                q[1]=q[2];
15                q[0]=q[1];
16            end
17    endmodule
```

	q[3]	q[2]	q[1]	q[0]
initial	1	0	0	1
1 st statement	1	0	0	1
2 nd statement	1	1	0	1
3 rd statement	1	1	1	1
4 th statement	1	1	1	1

All of these happened within one cycle!



 Procedural Assignment Statements (Blocking)



Thank you!
